

# EM NOISE & INTERFERENCE IN MEASUREMENT SETUPS

**Tools for Physicists 2025**


14.05.2025

**Matthias Hoek**


# DISCLAIMER

- What this is not...
  - Teaching design principles
  - Silver bullet for your measurement problems
- but rather...
  - Discussing possible reasons
  - Giving hints for solutions
  - Help with checking your setup

# MODEL OF INTERFERENCE INFLUENCE

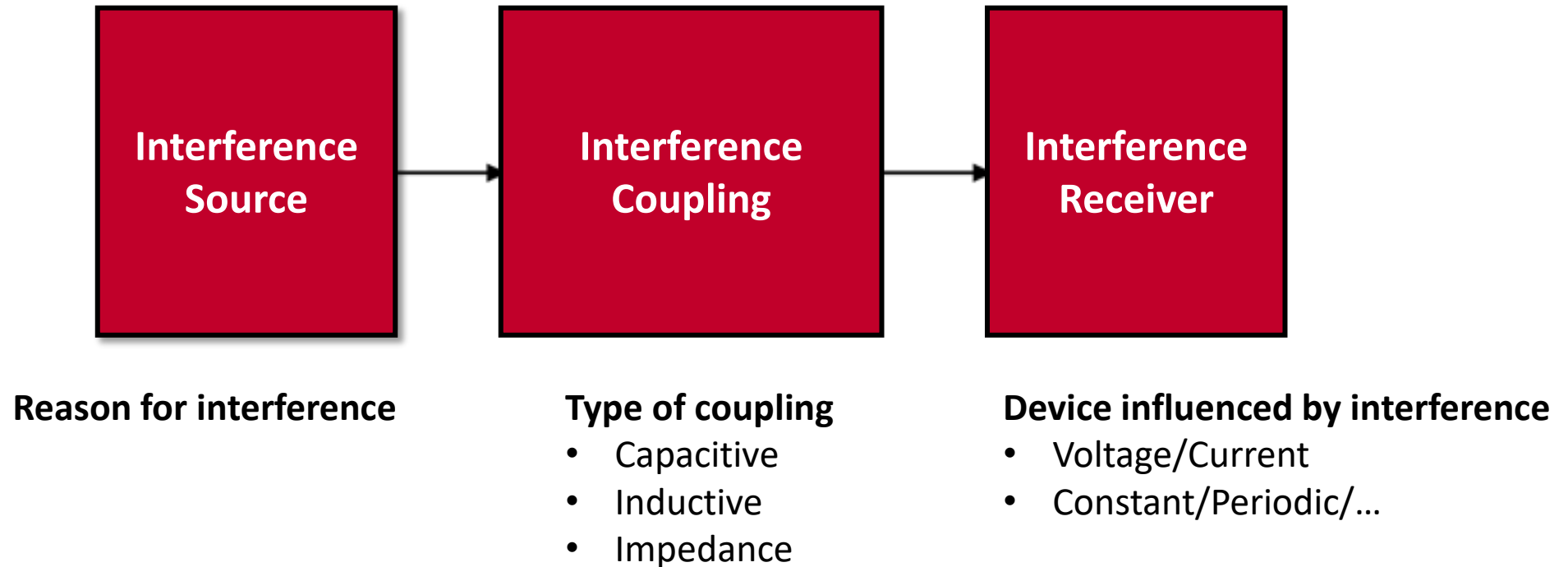


# SIGNAL TRANSMISSION

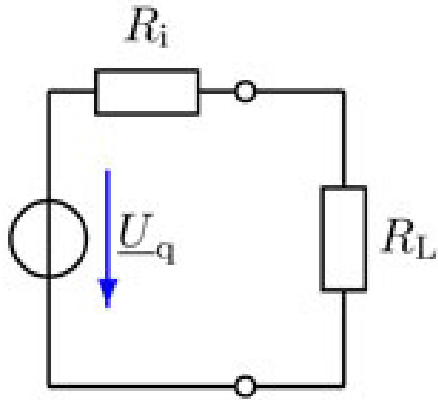

- Voltage


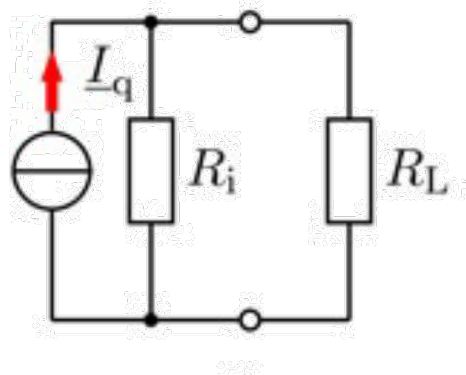
- In general:  $R_L \gg R_i$
- Current determined by  $R_L$ 
  - Can be ignored for large  $R_L$



- Current


- In general:  $R_L \ll R_i$
- Voltage determined by  $R_L$ 
  - Can be ignored for  $R_L \rightarrow 0$
- Example: PMT

# SIGNAL TRANSMISSION

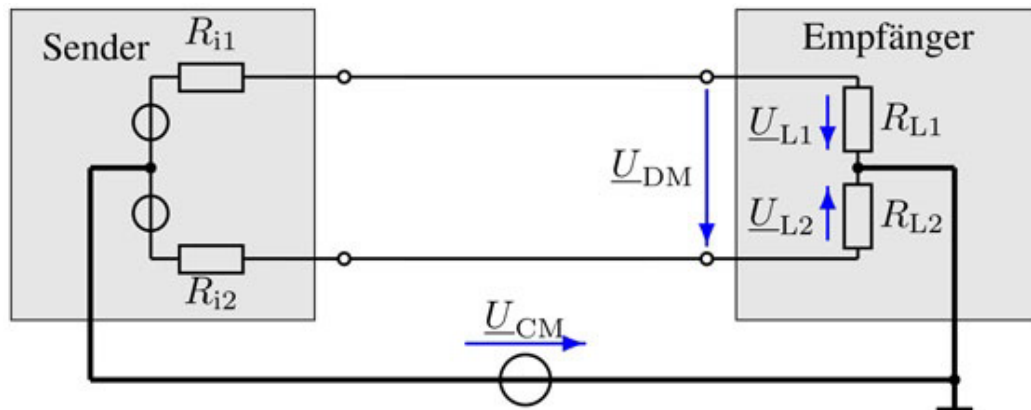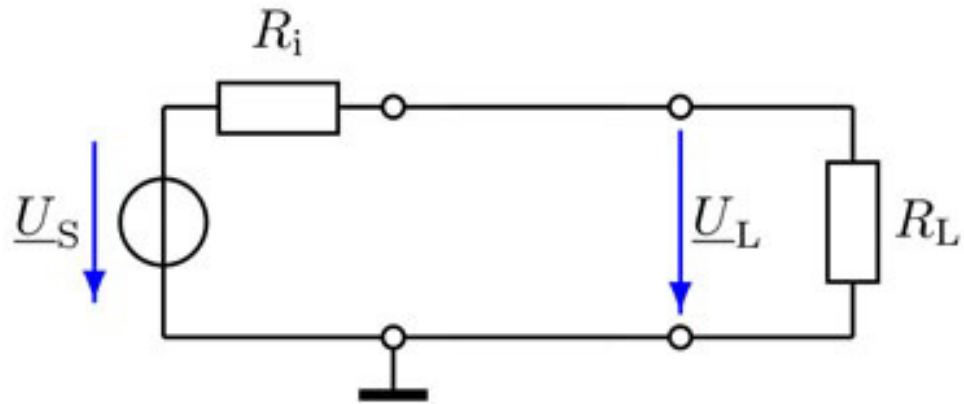

- Loop is always closed
  - Signal current has a return path!
- Asymmetric
  - One conductor connected to ground
- Symmetric
  - Signals symmetric wrt ground
  - Opposite polarity
  - Better in terms of interference

# SIGNAL TRANSMISSION – CABLE ROUTING

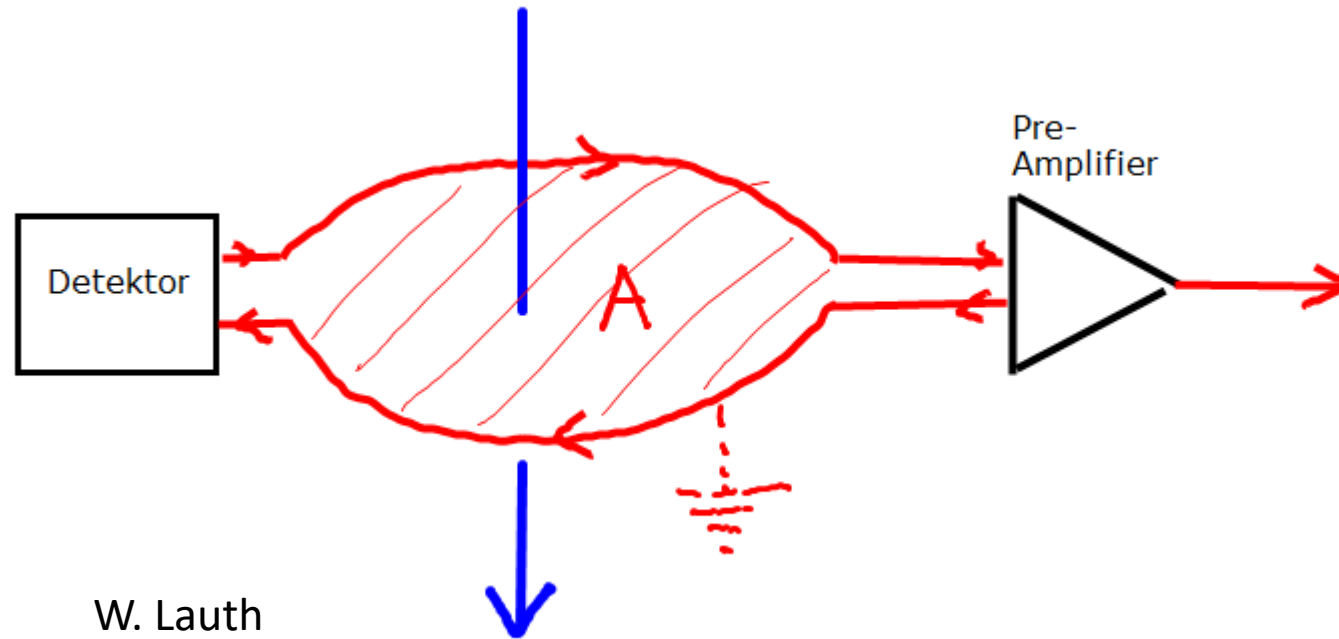

W. Lauth

Keep area between wires as small as possible!

- Example: Radio Transmitter (100MHz)


$$E \cong 100 \frac{\mu V}{m} \Rightarrow B = \frac{E}{c}$$
$$= 3.3 \cdot 10^{-13} \frac{Vs}{m^2}$$
$$|U_{ind}| = \frac{\partial B}{\partial t} \cdot A = 3 \cdot 10^{-5} \frac{V}{m^2} \cdot A$$

With  $A = 1m^2$  you get

$$|U_{ind}| = 30\mu V$$

But if transmitter is closer...

# GROUND/EARTH


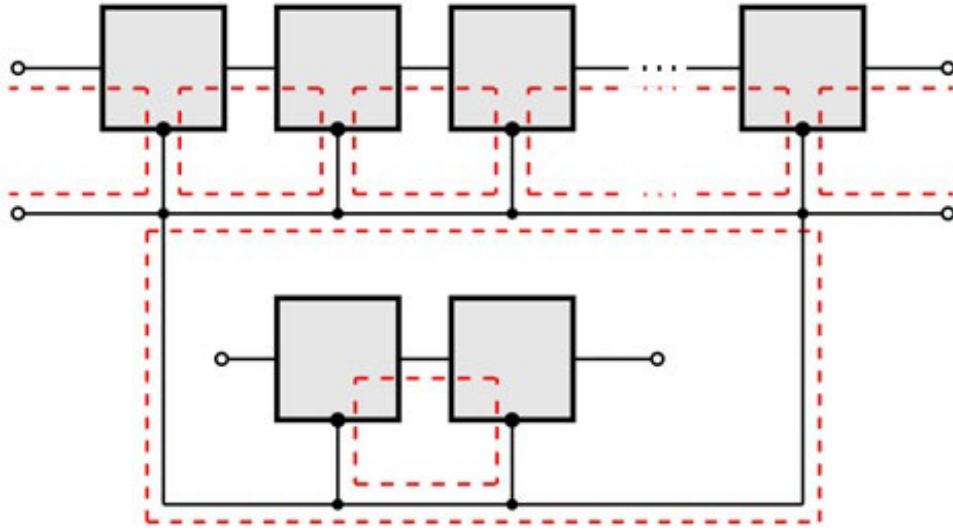


Devices connected in rows (typical lab setup)

- Two main tasks
  - 1) Reference potential
  - 2) Equalize potential
- Can lead to substantial currents
  - Bad for task 1)
- (Unwanted) Coupling of different loops

# INTERFERENCE COUPLING - CAPACITIVE


Asymmetric transmission

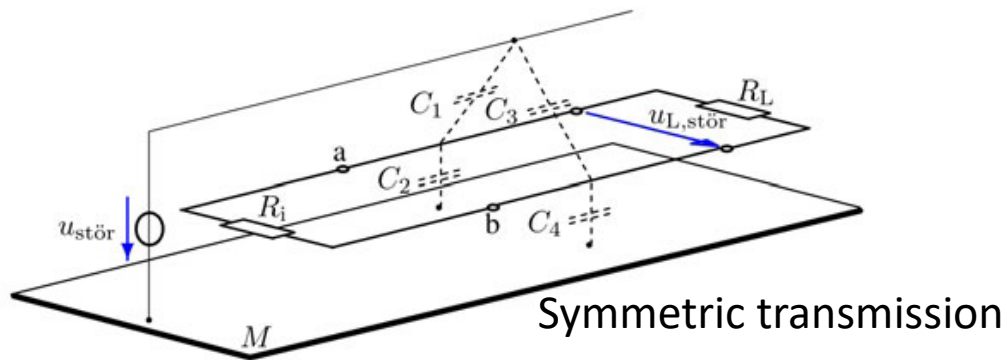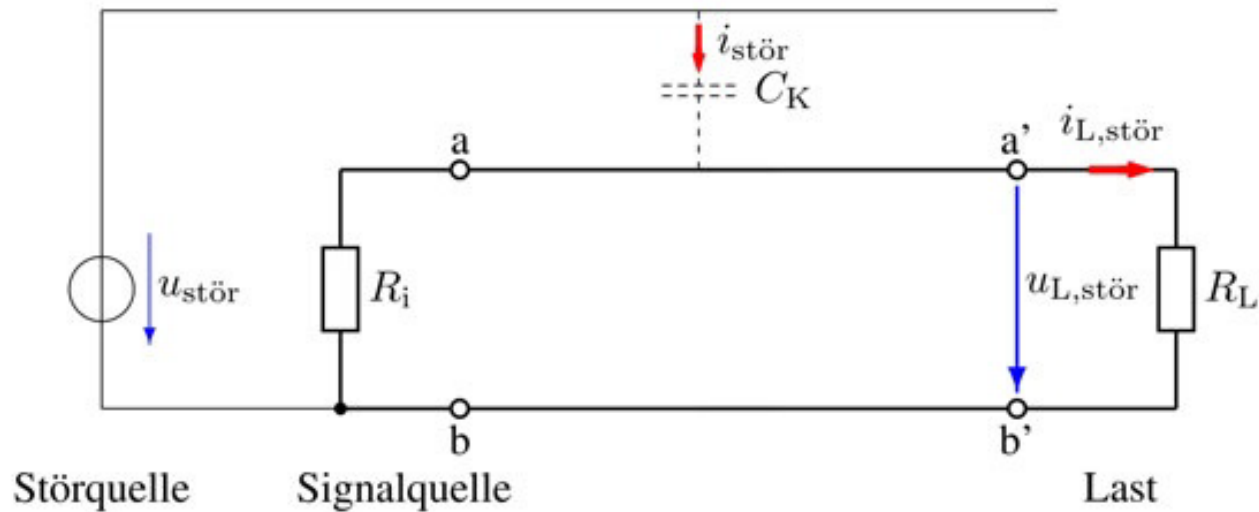

- Coupling via capacitance  $C_K$ 
  - <https://www.emissoftware.com/calculator/wire-over-ground-plane-capacitance/>
- $I_{IF} = C_K \frac{dU_{IF}}{dt}$ 
  - Depends on frequency
- $U_{L,IF} = C_K \frac{dU_{IF}}{dt} \frac{R_i \cdot R_L}{R_i + R_L}$
- Countermeasures
  - Reduce  $C_K, \frac{dU_{IF}}{dt}$
  - Use low-pass filter




# INTERFERENCE COUPLING - INDUCTIVE

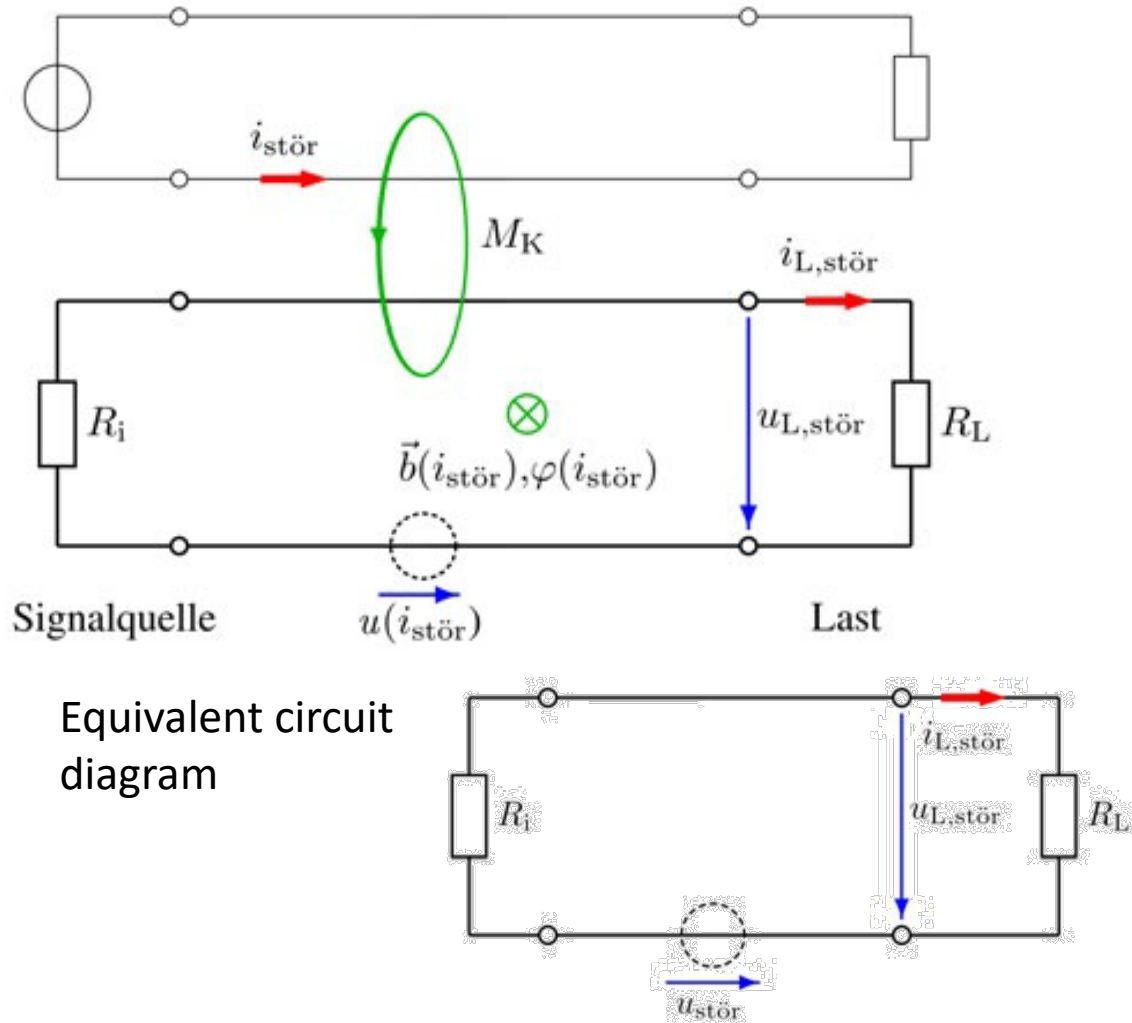


- Mutual inductance  $M_K$  reason for coupling
- $U_{IF} = M_K \frac{dI_{IF}}{dt} \approx U_{L,IF}$ 
  - Depends on frequency
- Countermeasures
  - Reduce coupling  $M_K$
  - Use current transmission
  - Reduce  $\frac{dI_{IF}}{dt}$

# INTERFERENCE COUPLING - INDUCTIVE

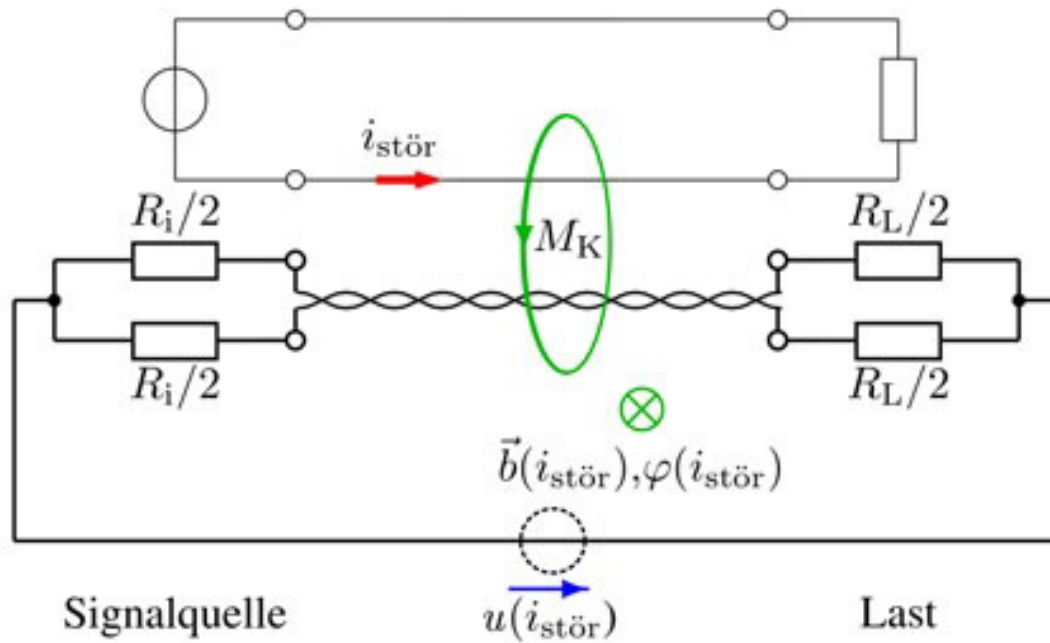


- Countermeasures cnt'd
  - Twisting transmission lines
    - Causes change of sign for magnetic flux
    - Still influence between neighbouring lines
  - Use low-pass filter

# INTERFERENCE COUPLING - IMPEDANCE

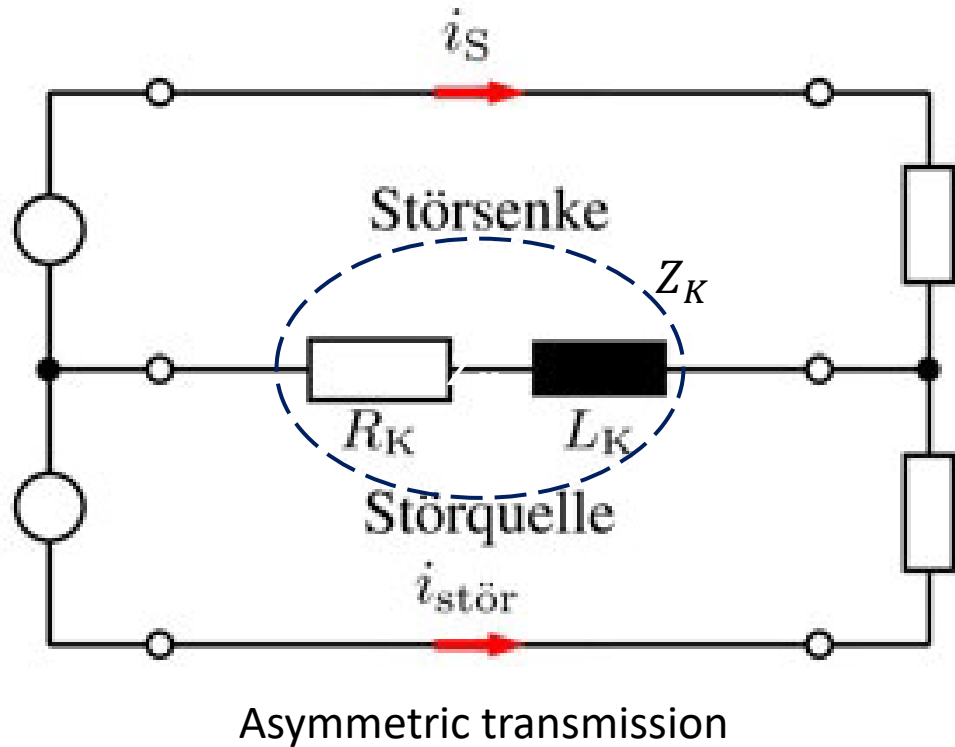

- Coupling through common impedance  $Z_K$ 
  - Often a common ground connection
- Different reference potentials
  - $U_{IF} = R_K \cdot I_{IF} + L_K \frac{dI_{IF}}{dt}$
- Minimize  $Z_K$ ,  $I_{IF}$ , and  $\frac{dI_{IF}}{dt}$




# INTERFERENCE COUPLING - IMPEDANCE

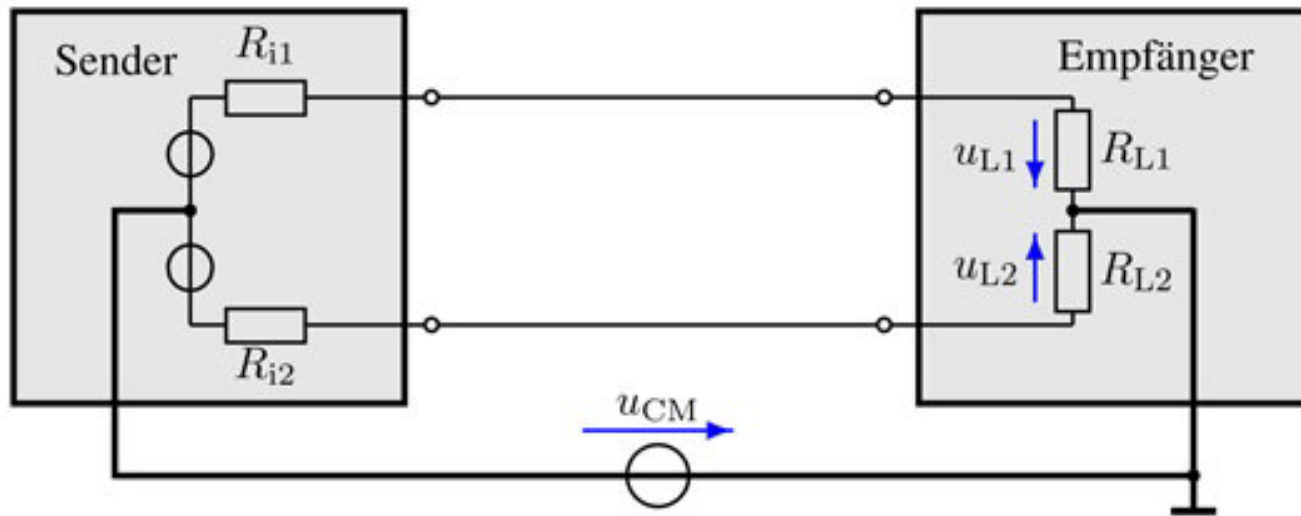

Symmetric transmission


- Only common-mode interference signal
- Reduces coupling to other loops
  - Compensates current on ground line
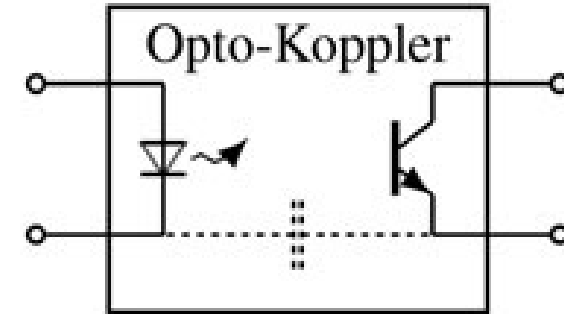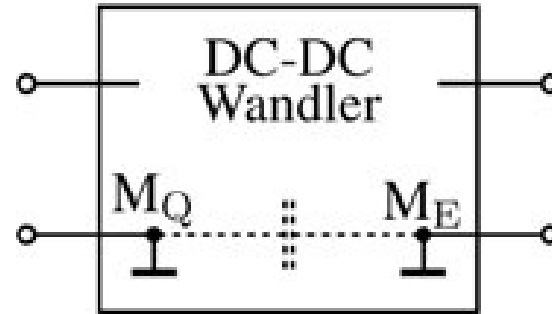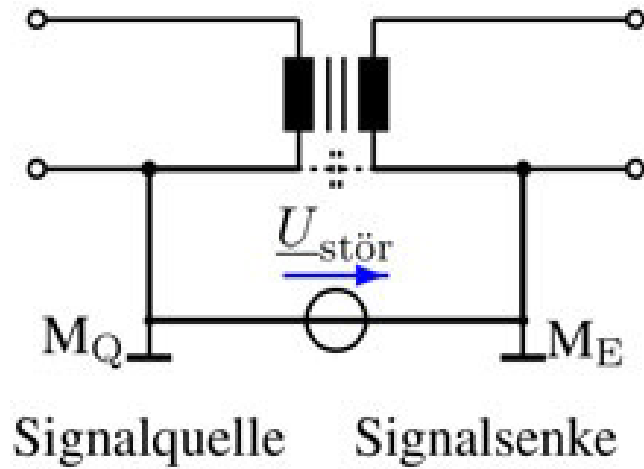
# COUNTER MEASURES IN THE LAB - ISOLATING TRANSFORMER





- Insert large resistance between different grounds
  - Decoupling (especially at low frequency)
- Might not be fast enough for some signals
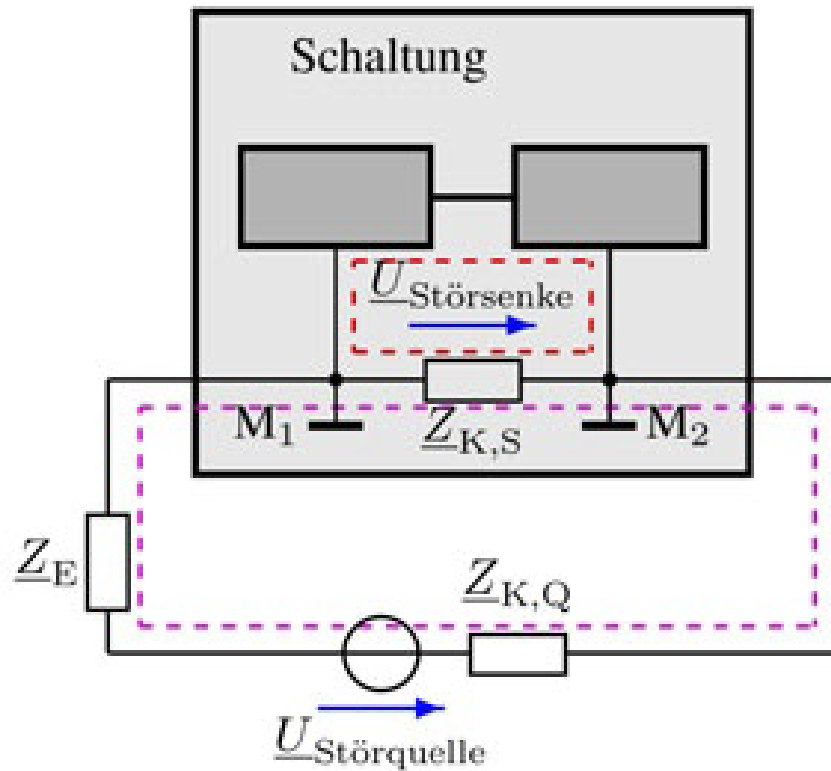
# COUNTER MEASURES IN THE LAB – GROUND LOOPS



- Multiple connections to ground in one circuit
  - Can be connected via a capacitance
- $Z_K$  define the coupling of the interference
  - Keep  $Z_K$  small
- $Z_E$  decouples interference
  - Make  $Z_E$  large
- Improve grounding scheme


# COUNTER MEASURES – GROUND CONNECTIONS

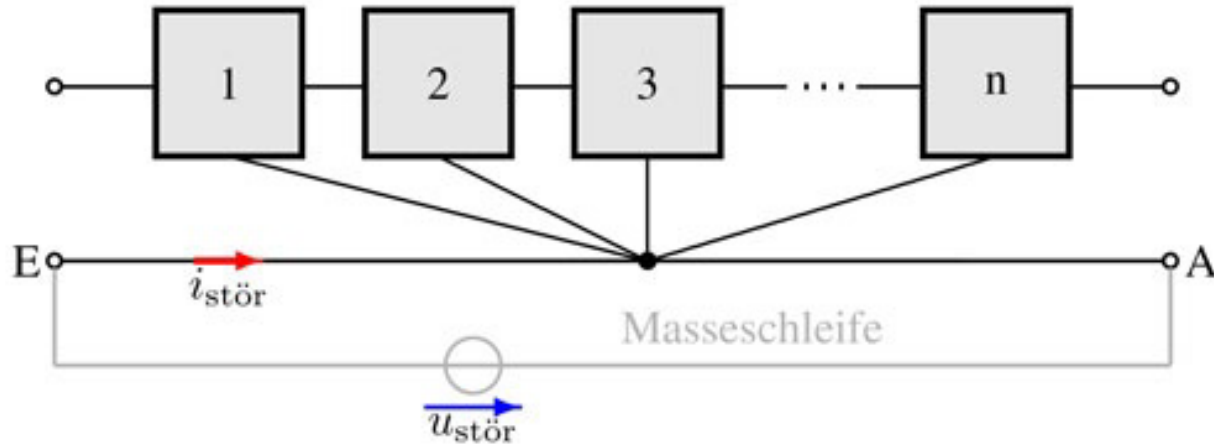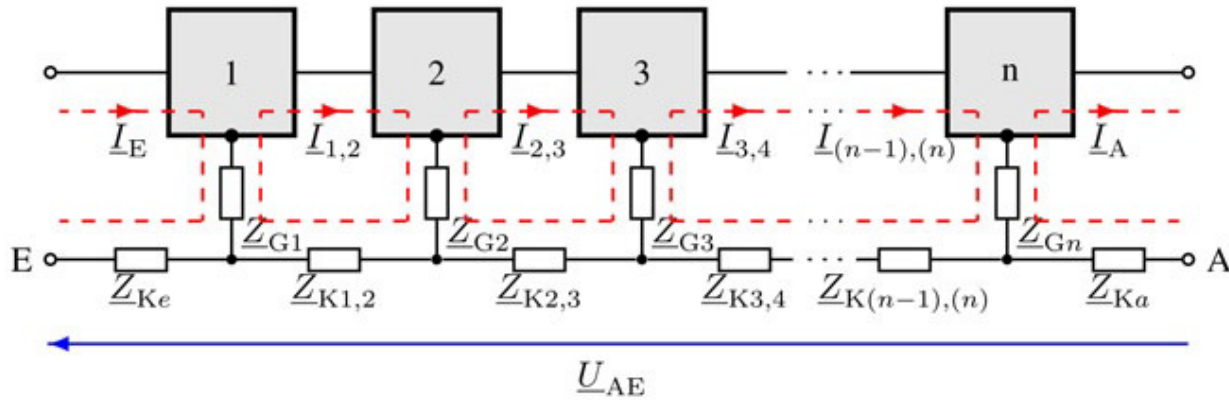

- Use one common connection to ground
  - No coupling from external ground loop
  - Impedance between stages is zero
- Might enhance coupling between different stages
  - Oscillations?


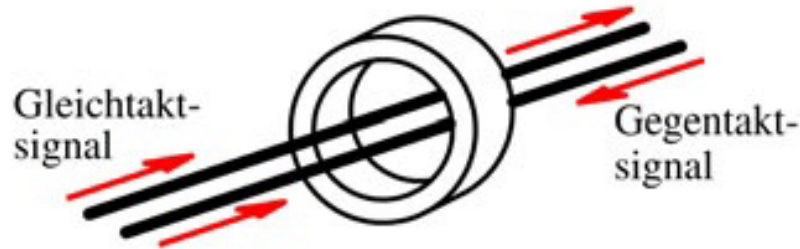
# COUNTER MEASURES - COMMON MODE CHOKE (GLEICHTAKTDROSSEL)



<https://commons.wikimedia.org/w/index.php?curid=5107944>

- Only common-mode signal has net current
- Ground loops have low impedance
  - Improvement already with small change of impedance
- Can also be used for multiple wires, e.g. flat-ribbon



# COUNTER MEASURES – FLAT RIBBON CABLE


SSSSSSSSS┐  
●●●●●●●●●●

S┐SS┐SS┐S  
●●●●●●●●●●

┐S┐S┐S┐S┐  
●●●●●●●●●●


- Keep loop area small
  - Reduce inductance
- More ground connections reduce resistance
  - Less voltage drop
- Twisted line pairs

# COUNTER MEASURES – CABLE CONNECTIONS

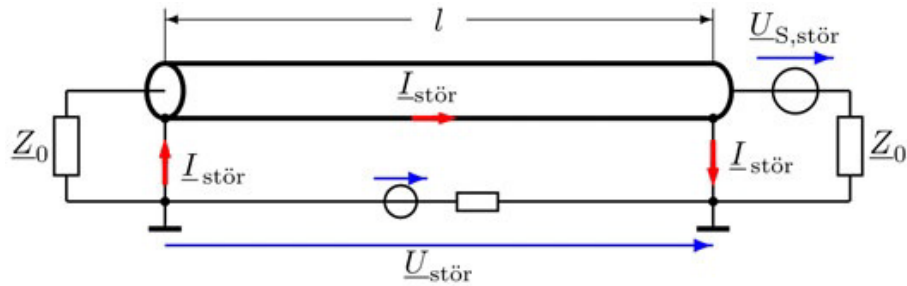


- Capacitive and EM coupling can be suppressed by screen
- Current  $I_{IF}$  in screen can cause interference  $U_{S,IF}$
- Braided screen
  - Magnetic field inside screen  $\neq 0$
  - Inductance
- Keep connection impedance low

# COUNTER MEASURES – CABLE CONNECTIONS

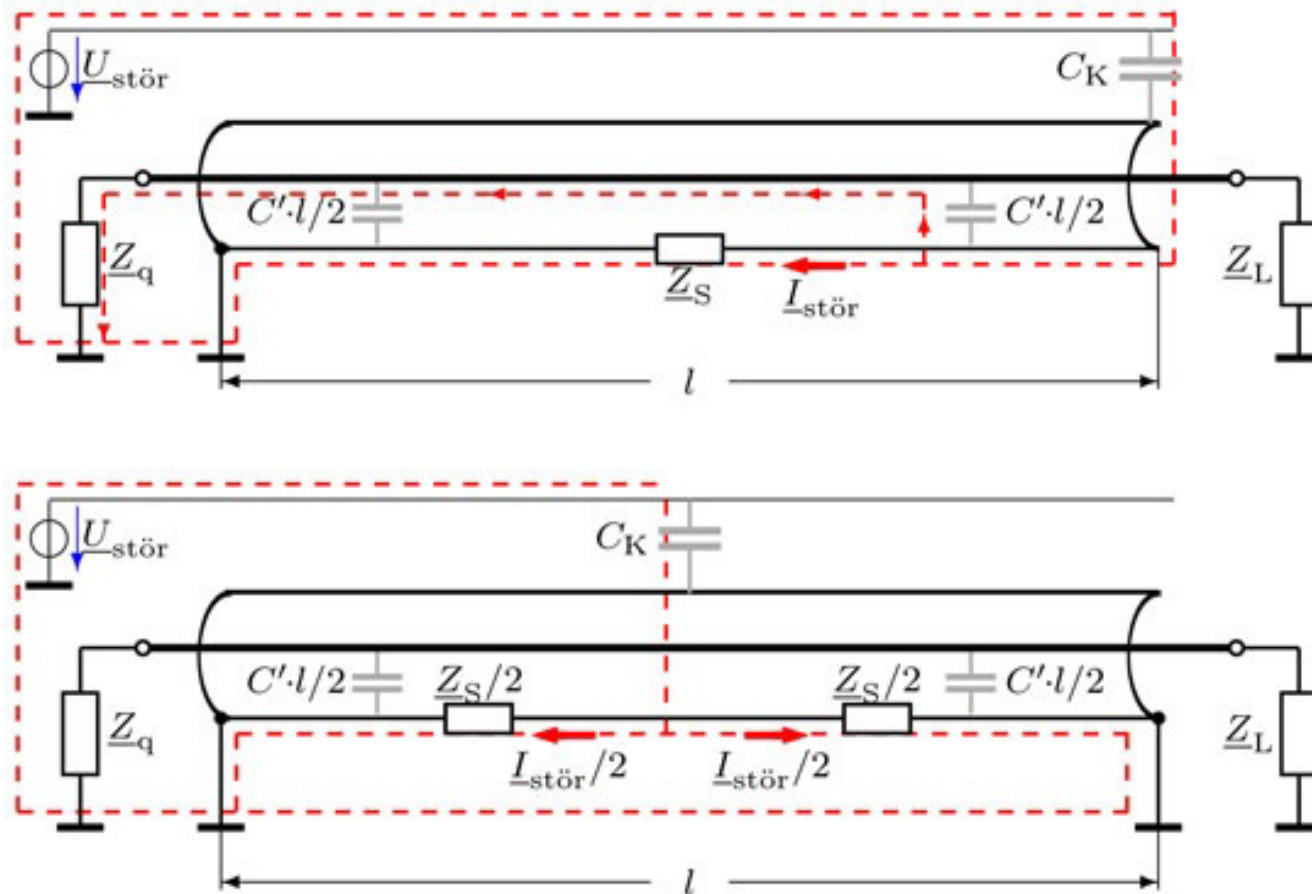

- Capacitive coupling
- One-sided ground connection
  - Induced potential causes noise on signal line
- Two-sided ground connection
  - Both branches (partially) compensate

# COUNTER MEASURES – CABLE CONNECTIONS

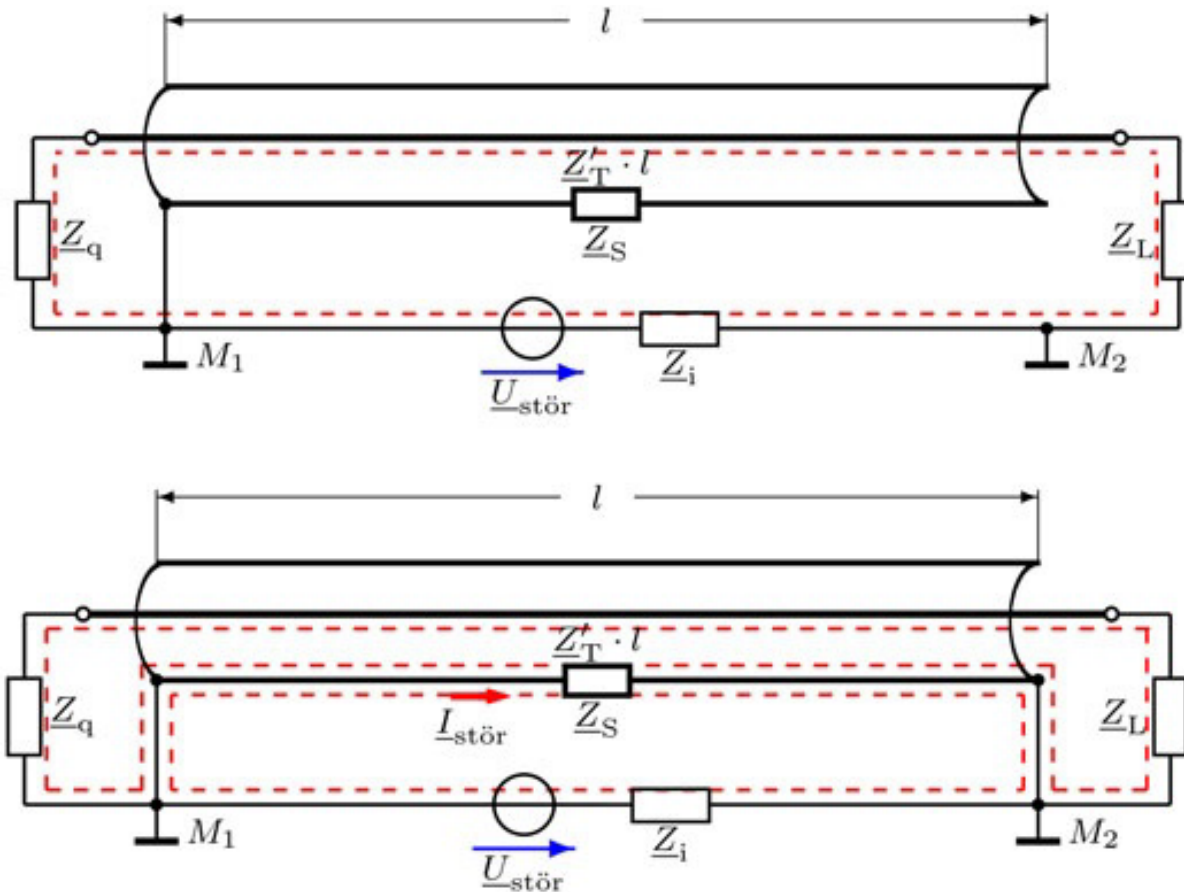

- Inductive or impedance coupling
- One-sided ground connection
  - $U_{IF}$  directly superimposed on signal!
- Two-sided ground connection
  - Only partially superimposed ( $\frac{Z'_T \cdot l}{Z_S}$ )

# FINDING THE SOURCES – MAY BE?

- Capacitive Coupling

- Short signal source ( $R_i = 0$ )
  - Interference should vanish

- Inductive Coupling

- Open signal source ( $R_i \rightarrow \infty$ )
  - Interference should vanish (but gets larger if capacitive)
  - True also for impedance coupling
- Shielding
  - Do not ground (capacitive coupling)